CHAPTER 12 (Odd)

1.
$$e = N \frac{d\phi}{dt} = (50 \text{ t})(0.085 \text{ Wb/s}) = 4.25 \text{ V}$$

3.
$$N = \frac{e_{\text{ind}}}{\frac{d\phi}{dt}} = \frac{42 \text{ mV}}{3 \times 10^{-3} \text{ Wb/s}} = 14 \text{ turns}$$

5.
$$d = 0.25 \text{ jnf.} \left[\frac{1 \text{ m}}{39.37 \text{ jnf.}} \right] = 6.35 \text{ mm}$$

$$A = \frac{\pi d^2}{4} = \frac{(3.14)(6.35 \times 10^{-3} \text{ m})^2}{4} = 31.65 \times 10^{-6} \text{ m}^2$$

$$\ell = 4 \text{ jnf.} \left[\frac{1 \text{ m}}{39.37 \text{ jnf.}} \right] = 0.1016 \text{ m}$$

$$L = \frac{N^2 \mu_r \mu_o A}{\ell} = \frac{(200 \text{ t})^2 (1)(4\pi \times 10^{-7})(31.65 \times 10^{-6} \text{ m}^2)}{0.1016 \text{ m}} = 15.65 \mu\text{H}$$

7. a.
$$e_L = L \frac{di}{dt} = (5 \text{ H})(0.5 \text{ A/s}) = 2.5 \text{ V}$$

b.
$$e_L = (5 \text{ H})(60 \times 10^{-3} \text{ A/s}) = 0.3 \text{ V}$$

c.
$$e_L = (5 \text{ H})(0.04 \times 10^3 \text{ A/s}) = 200 \text{ V}$$

9.
$$e_L = L \frac{\Delta i}{\Delta t}$$
: 0 - 3 ms, $e_L = 0$ V

$$3 - 8 \text{ ms}, e_L = (200 \text{ mH}) \left[\frac{40 \times 10^{-3} \text{ A}}{5 \times 10^{-3} \text{ s}} \right] = 1.6 \text{ V}$$


$$8 - 13 \text{ ms}, e_L = -(200 \text{ mH}) \left[\frac{40 \times 10^{-3} \text{ A}}{5 \times 10^{-3} \text{ s}} \right] = -1.6 \text{ V}$$

$$13 - 14 \text{ ms}, e_L = 0 \text{ V}$$

$$14 - 15 \text{ ms}, e_L = (200 \text{ mH}) \left[\frac{40 \times 10^{-3} \text{ A}}{5 \times 10^{-3} \text{ s}} \right] = 8 \text{ V}$$

$$15 - 16 \text{ ms}, e_L = -8 \text{ V}$$
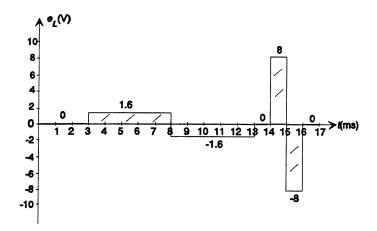
$$16 - 17 \text{ ms}, e_L = 0 \text{ V}$$



11.
$$L = 10 \text{ mH}, 4 \text{ mA at } t = 0 \text{ s}$$

$$v_L = L \frac{\Delta i}{\Delta t} \Rightarrow \Delta i = \frac{\Delta t}{L} v_L$$


$$0-5 \mu s$$
: $v_L = 0 \text{ V}$, $\Delta i_L = 0 \text{ mA}$ and $i_L = 4 \text{ mA}$

$$5 - 10 \ \mu s$$
: $\Delta i_L = \frac{5 \ \mu s}{10 \ \text{mH}} (-24 \ \text{V}) = -12 \ \text{mA}$

$$10 - 12 \mu s$$
: $\Delta i_L = \frac{2 \mu s}{10 \text{ mH}} (+60 \text{ V}) = +12 \text{ mA}$

12 - 16
$$\mu$$
s: $v_L = 0$ V, $\Delta i_L = 0$ mA and $i_L = 4$ mA
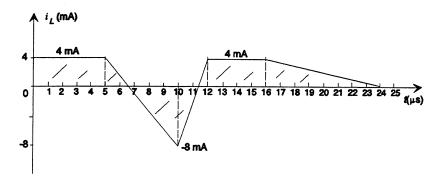
$$16 - 24 \mu s$$
: $\Delta i_L = \frac{8 \mu s}{10 \text{ mH}} (-5 \text{ V}) = -4 \text{ mA}$



13. a.
$$\tau = \frac{L}{R} = \frac{5 \text{ mH}}{2.2 \text{ k}\Omega} = 2.27 \text{ }\mu\text{s}$$


b.
$$i_L = \frac{E}{R}(1 - e^{-t/\tau}) = \frac{12 \text{ V}}{2.2 \text{ k}\Omega}(1 - e^{-t/\tau}) = 5.45 \times 10^{-3}(1 - e^{-t/2.27 \mu s})$$

c.
$$v_L = Ee^{-t/\tau} = 12e^{-t/2.27 \,\mu s}$$

 $v_R = i_R R = i_L R = E(1 - e^{-t/\tau}) = 12(1 - e^{-t/2.27 \,\mu s})$

d.
$$i_L$$
: $1\tau = 3.45$ mA, $3\tau = 5.179$ mA, $5\tau = 5.413$ mA v_L : $1\tau = 4.415$ V, $3\tau = 0.598$ V, $5\tau = 0.081$ V

e.

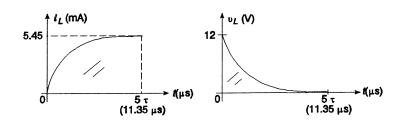

15. a.
$$\tau = \frac{L}{R} = \frac{120 \text{ mH}}{4.7 \text{ k}\Omega + 3.9 \text{ k}\Omega} = \frac{120 \text{ mH}}{8.6 \text{ k}\Omega} = 13.95 \text{ } \mu\text{s}$$

$$i_L = I_f + (I_i - I_f)e^{-t/T}$$

$$I_f = \frac{36 \text{ V}}{8.6 \text{ k}\Omega} = 4.186 \text{ mA}$$


$$i_L = 4.186 \text{ mA} + (8 \text{ mA} - 4.186 \text{ mA})e^{-t/13.95 \text{ } \mu\text{s}}$$

$$i_L = 4.186 \text{ mA} - 3.814 \text{ mA}e^{-t/13.95 \text{ } \mu\text{s}}$$

$$v_{R_T}(0+) = 8 \text{ mA}(8.6 \text{ k}\Omega) = 68.8 \text{ V}$$

KVL: $+36 \text{ V} - 68.8 \text{ V} - v_L = 0$,

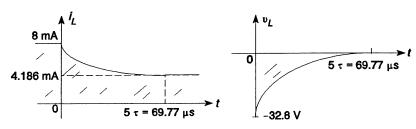 $v_L(0+) = 36 \text{ V} - 68.8 \text{ V} = -32.8 \text{ V}$
 $v_L = -32.8 \text{ V}e^{-t/13.95 \mu s}$




17. a.
$$\frac{10 \text{ k}\Omega}{10 \text{ k}\Omega} = 10 \text{ k}\Omega \qquad \tau = \frac{L}{R} = \frac{10 \text{ mH}}{10 \text{ k}\Omega} = 1 \text{ } \mu\text{s}$$

$$v_L = 20e^{-t/1 \mu s}, i_L = \frac{E}{R}(1 - e^{-t/\tau}) = 2 \times 10^{-3}(1 - e^{-t/1 \mu s})$$

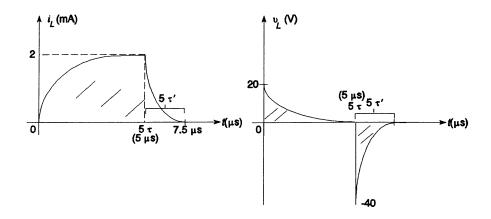b.
$$5\tau \Rightarrow$$
 steady state
$$\tau' = \frac{L}{R} = \frac{10 \text{ mH}}{20 \text{ k}\Omega} = 0.5 \text{ } \mu\text{s}$$

$$i_L = I_m e^{-t/\tau'} = 2 \times 10^{-3} e^{-t/0.5 \text{ } \mu\text{s}}$$

$$v_L = -(2 \text{ mA})(20 \text{ k}\Omega) e^{-t/\tau} = -40 e^{-t/0.5 \text{ } \mu\text{s}}$$



19. a.
$$\tau = \frac{L}{R} = \frac{1 \text{ mH}}{2 \text{ k}\Omega} = 0.5 \text{ } \mu\text{s}$$

$$i_L = \frac{E}{R} (1 - e^{-t/\tau}) = \frac{12 \text{ } V}{2 \text{ k}\Omega} (1 - e^{-t/\tau}) = 6 \times 10^{-3} (1 - e^{-t/0.5 \text{ } \mu\text{s}})$$

$$v_L = Ee^{-t/\tau} = 12e^{-t/0.5 \text{ } \mu\text{s}}$$
b.
$$i_L = 6 \times 10^{-3} (1 - e^{-t/0.5 \text{ } \mu\text{s}}) = 6 \times 10^{-3} (1 - e^{-1 \text{ } \mu\text{s}/0.5 \text{ } \mu\text{s}})$$

b.
$$i_L = 6 \times 10^{-3} (1 - e^{-t/0.5 \,\mu\text{s}}) = 6 \times 10^{-3} (1 - e^{-1 \,\mu\text{s}/0.5 \,\mu\text{s}})$$

$$= 6 \times 10^{-3} (1 - e^{-2}) = 5.188 \,\text{mA}$$

$$i_L = I'_m e^{-t/\tau'} \qquad \tau' = \frac{L}{R} = \frac{1 \,\text{mH}}{12 \,\text{k}\Omega} = 0.0833 \,\mu\text{s} = 83.3 \,\text{ns}$$


$$i_L = 5.188 \times 10^{-3} e^{-t/83.3 \,\text{ns}}$$

$$t = 1 \,\mu\text{s}: \ v_L = 12 e^{-t/0.5 \,\mu\text{s}} = 12 e^{-2} = 12 (0.1353) = 1.624 \,\text{V}$$

$$V'_L = (5.188 \,\text{mA}) (12 \,\text{k}\Omega) = 62.256 \,\text{V}$$

$$v_L = -62.256 e^{-t/83.3 \,\text{ns}}$$

c.

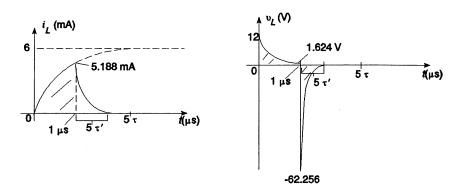

21.
$$2 \text{ mA} = 1.78 \text{ mA} + 2.22 \text{ mA} e^{-t/11.11 \mu s}$$

$$0.22 \text{ mA} = 2.22 \text{ mA} e^{-t/11.11 \mu s}$$

$$99.1 \times 10^{-3} = e^{-t/11.11 \mu s}$$

$$\log_e 99.1 \times 10^{-3} = \log_e (e^{-t/11.11 \mu s})$$

$$-2.312 = -t/11.11 \mu s$$

$$t = (11.11 \mu s)(2.312)$$

$$t = 25.68 \mu s$$

$$R_{Th} = 2.2 \text{ k}\Omega \| 4.7 \text{ k}\Omega = 1.498 \text{ k}\Omega$$

$$E_{Th} = \frac{4.7 \text{ k}\Omega(8 \text{ V})}{4.7 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 5.45 \text{ V}$$

$$\tau = \frac{L}{R} = \frac{10 \text{ mH}}{1.498 \text{ k}\Omega} = 6.676 \text{ }\mu\text{s}$$

$$i_L = \frac{E}{R}(1 - e^{-t/\tau}) = \frac{5.45 \text{ V}}{1.498 \text{ k}\Omega}(1 - e^{-t/\tau}) = 3.638 \times 10^{-3}(1 - e^{-t/6.676 \,\mu\text{s}})$$


$$v_L = Ee^{-t/\tau} = 5.45e^{-t/6.676 \,\mu\text{s}}$$


b.
$$t = 10 \ \mu s$$
:
 $i_L = 3.638 \times 10^{-3} (1 - e^{-10 \ \mu s/6.676 \ \mu s}) = 3.638 \times 10^{-3} (1 - e^{-1.4})$
 $= 2.825 \ \text{mA}$
 $v_L = 5.45(0.2236) = 1.2186 \ \text{V}$

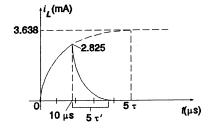c.
$$\tau' = \frac{L}{R} = \frac{10 \text{ mH}}{4.7 \text{ k}\Omega} = 2.128 \text{ }\mu\text{s}$$

 $i_L = 2.825 \times 10^{-3} e^{-t/2.128 \text{ }\mu\text{s}}$

At
$$t = 10 \ \mu s$$
:
 $V_L = (2.825 \ \text{mA})(4.7 \ \text{k}\Omega) = 13.278 \ \text{V}$
 $v_L = -13.278 e^{-t/2.128 \ \mu s}$



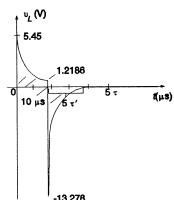

25. a.
$$v_L = Ee^{-t/\tau}$$
 $\tau = \frac{L}{R_1 + R_3} = \frac{0.6 \text{ H}}{100 \Omega + 20 \Omega} = \frac{0.6 \text{ H}}{120 \Omega} = 5 \text{ ms}$

$$v_L = 36 e^{-t/5 \text{ ms}}$$

$$v_L = 36 e^{-25 \text{ ms/5 ms}} = 36 e^{-5} = 36(0.00674) = \mathbf{0.243 V}$$

b.
$$v_L = 36 e^{-1 \text{ ms/5 ms}} = 36 e^{-0.2} = 36(0.819) = 29.47 \text{ V}$$

c.
$$v_{R_1} = i_{R_1}R_1 = i_LR_1 = \left[\frac{E}{R_1 + R_3}(1 - e^{-t/7})\right]R_1$$

$$= \left[\frac{36 \text{ V}}{120 \Omega}(1 - e^{-t/5 \text{ ms}})\right]100 \Omega$$

$$= (300 \text{ mA}(1 - e^{-t/5 \text{ ms}}))100 \Omega$$

$$= 30 \text{ V}(1 - e^{-5 \text{ ms}/5 \text{ ms}}) = 30 \text{ V}(1 - e^{-1})$$

$$= 30 \text{ V}(1 - 0.368) = 18.96 \text{ V}$$

d.
$$i_{L} = 300 \text{ mA} (1 - e^{-t/5 \text{ ms}})$$

$$100 \text{ mA} = 300 \text{ mA} (1 - e^{-t/5 \text{ ms}})$$

$$0.333 = 1 - e^{-t/5 \text{ ms}}$$

$$0.667 = e^{-t/5 \text{ ms}}$$

$$\log_{e} 0.667 = -t/5 \text{ ms}$$

$$0.405 = t/5 \text{ ms}$$

$$t = 0.405(5 \text{ ms}) = 2.025 \text{ ms}$$

27. $L \Rightarrow$ open circuit equivalent a.

$$V_L = \frac{10 \text{ M}\Omega(24 \text{ V})}{10 \text{ M}\Omega + 2 \text{ M}\Omega} = 20 \text{ V}$$

$$I_{L_{\text{final}}} = \frac{E_{Th}}{R_{Th}} = \frac{20 \text{ V}}{1.667 \text{ M}\Omega} = 12 \mu\text{A}$$

c.
$$i_L = 12 \ \mu \text{A} (1 - e^{-t/3} \ \mu \text{s}) \qquad \tau = \frac{L}{R} = \frac{5 \ \text{H}}{1.667 \ \text{M}\Omega} = 3 \ \mu \text{s}$$

$$10 \ \mu \text{A} = 12 \ \mu \text{A} (1 - e^{-t/3} \ \mu \text{s})$$

$$0.8333 = 1 - e^{-t/3} \ \mu \text{s}$$

$$0.1667 = e^{-t/3} \ \mu \text{s}$$

$$10g_e(0.1667) = -t/3 \ \mu \text{s}$$

$$1.792 = t/3 \ \mu \text{s}$$

$$t = 1.792(3 \ \mu \text{s}) = 5.376 \ \mu \text{s}$$

d.
$$v_L = 20e^{-t/3} \,\mu\text{s} = 20e^{-12} \,\mu\text{s}/3 \,\mu\text{s} = 20e^{-4}$$

= 20(0.0183) = **0.366** V

29. a.
$$I_i = -\frac{24 \text{ V}}{2.2 \text{ k}\Omega} = -10.91 \text{ mA}$$

Switch open:
$$I_f = -\frac{24 \text{ V}}{2.2 \text{ k}\Omega + 4.7 \text{ k}\Omega} = -\frac{24 \text{ V}}{6.9 \text{ k}\Omega} = -3.478 \text{ mA}$$

$$i_L = I_f + (I_i - I_f)e^{-t/\tau}$$

$$\tau = \frac{L}{R} = \frac{1.2 \text{ H}}{6.9 \text{ k}\Omega} = 173.9 \text{ }\mu\text{s}$$


$$i_L = -3.478 \text{ mA} + (-10.91 \text{ mA} - (-3.478 \text{ mA}))e^{-t/173.9 \text{ }\mu\text{s}}$$

$$i_L = -3.478 \text{ mA} - 7.432 \text{ mA}e^{-t/173.9 \text{ }\mu\text{s}}$$

$$t = 0+:$$
 $-75.28 \text{ V}+$
 $v_L = 51.28 \text{ V}e^{-t/173.9 \mu}$

$$v_R(0+) = (10.91 \text{ mA})(6.9 \text{ k}\Omega) = 75.28 \text{ V}$$

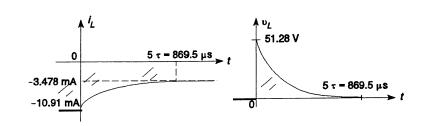KVL: $-24 \text{ V} + 75.28 \text{ V} - v_L = 0$
 $v_L = 51.28 \text{ V}$



31. a.
$$L_T = 4 H + 2 H + 3 H \| 6 H = 8 H$$

b.
$$L_T = 12 \text{ H} \| (3.6 \text{ H} + 4 \text{ H} \| 6 \text{ H}) = 12 \text{ H} \| 6 \text{ H} = 4 \text{ H}$$

33.
$$L'_T = 6 H \| (1 H + 2 H) = 6 H \| 3 H = 2 H$$

35.
$$I_1 = \frac{16 \text{ V}}{4 \text{ k}\Omega + 0} = 4 \text{ mA}, V_1 = 16 \text{ V}, V_2 = 0 \text{ V}$$

37.
$$V_{1} = \frac{(3 \Omega + 3\Omega \| 6 \Omega)(50 \text{ V})}{(3 \Omega + 3 \Omega \| 6\Omega) + 20 \Omega} = \frac{(3 \Omega + 2 \Omega)(50 \text{ V})}{(3 \Omega + 2 \Omega) + 20 \Omega} = \mathbf{10 V}$$

$$R_{T} = 20 \Omega + 3 \Omega + 3 \Omega \| 6 \Omega = 23 \Omega + 2 \Omega = 25 \Omega$$

$$I_{S} = I_{1} = \frac{50 \text{ V}}{25 \Omega} = \mathbf{2 A}$$

$$I_{5\Omega} = 0 \text{ A}, \ \therefore \ I_2 = \frac{6 \ \Omega(I_s)}{6 \ \Omega + 3 \ \Omega} = \frac{6 \ \Omega(2 \ \text{A})}{6 \ \Omega + 3 \ \Omega} = 1.33 \ \text{A}$$

39.
$$W_{5\mu F} = \frac{1}{2}CV^2 = \frac{1}{2}(5 \ \mu F)(12 \ V)^2 = 360 \ \mu J$$

$$W_{6H} = \frac{1}{2}LI^2 = \frac{1}{2}(6 \text{ H})(2 \text{ A})^2 = 12 \text{ J}$$

CHAPTER 12 (Even)

2.
$$e = N \frac{d\phi}{dt} \Rightarrow \frac{d\phi}{dt} = \frac{e}{N} = \frac{20 \text{ V}}{40 \text{ t}} = 0.5 \text{ Wb/s}$$

4.
$$A = \frac{\pi d^2}{4} = \frac{\pi (5 \text{ mm})^2}{4} = 19.625 \times 10^{-6} \text{ m}^2$$

$$L = \frac{N^2 \mu A}{\ell} = \frac{(200 \text{ t})^2 (4\pi \times 10^{-7})(19.625 \times 10^{-6} \text{ m}^2)}{0.075 \text{ m}} = 13.146 \mu\text{H}$$


6. a.
$$L = \frac{N^2 \mu A}{\ell} = \frac{(300 \text{ t})^2 (4\pi \times 10^{-7})(1.5 \times 10^{-4} \text{ m}^2)}{0.1 \text{ m}} = 169.56 \ \mu\text{H}$$

b.
$$L = \mu_r L_o = (2 \times 10^3)(169.56 \,\mu\text{H}) = 339.12 \,\text{mH}$$

8.
$$e_L = L\frac{di}{dt} = (50 \text{ mH}) \left[\frac{0.1 \times 10^{-3} \text{ A}}{10^{-6} \text{ s}} \right] = 5 \text{ V}$$

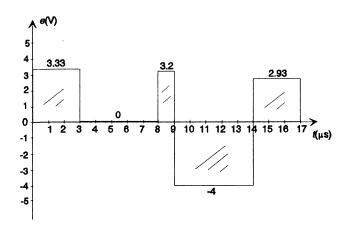10.
$$e = L \frac{\Delta i}{\Delta t} = (0.2 \text{ H}) \frac{\Delta i}{\Delta t}$$

 $0 - 3 \mu \text{s}: e = (0.2 \text{ H}) \left[\frac{50 \mu \text{A}}{3 \mu \text{s}} \right] = 3.33 \text{ V}$
 $3 - 8 \mu \text{s}: e = (0.2 \text{ H})(0) = 0 \text{ V}$
 $8 - 9 \mu \text{s}: e = (0.2 \text{ H}) \left[\frac{16 \mu \text{A}}{1 \mu \text{s}} \right] = 3.2 \text{ V}$
 $9 - 14 \mu \text{s}: e = -(0.2 \text{ H}) \left[\frac{100 \mu \text{A}}{5 \mu \text{s}} \right] = -4 \text{ V}$
 $14 - 17 \mu \text{s}: e = (0.2 \text{ H}) \left[\frac{44 \mu \text{A}}{3 \mu \text{s}} \right] = 2.93 \text{ V}$



12. a.
$$\tau = \frac{L}{R} = \frac{250 \text{ mH}}{20 \text{ k}\Omega} = 12.5 \text{ } \mu\text{s}$$

b.
$$i_L = \frac{E}{R}(1 - e^{-t/\tau}) = \frac{40 \text{ mV}}{20 \text{ k}\Omega}(1 - e^{-t/\tau})$$


= $2 \times 10^{-6}(1 - e^{-t/12.5 \,\mu\text{s}})$


c.
$$v_L = Ee^{-t/\tau} = 40 \times 10^{-3} e^{-t/12.5 \,\mu s}$$

 $v_R = i_R R = i_L R = E(1 - e^{-t/\tau}) = 40 \times 10^{-3} (1 - e^{-t/12.5 \,\mu s})$


d.
$$i_L$$
: $1\tau = 1.264 \mu A$, $3\tau = 1.9 \mu A$, $5\tau = 1.987 \mu A$
 v_L : $1\tau = 14.72 \text{ V}$, $3\tau = 1.99 \text{ V}$, $5\tau = 0.2695 \text{ V}$

e.

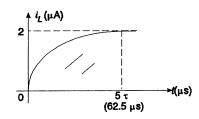

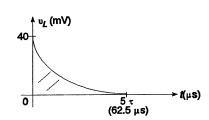

14. a. Source conversion:

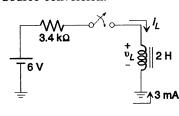


$$\tau = \frac{L}{R} = \frac{2 \text{ H}}{3.4 \text{ k}\Omega} = 588.2 \text{ } \mu\text{s}$$

$$i_L = I_f + (I_i - I_f)e^{-t/\tau}$$

$$I_f = \frac{6 \text{ V}}{3.4 \text{ k}\Omega} = 1.765 \text{ mA}$$


$$i_L = 1.765 \text{ mA} + (-3 \text{ mA} - 1.765 \text{ mA})e^{-t/588.2 \text{ } \mu\text{s}}$$

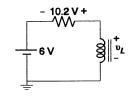
$$i_L = 1.765 \text{ mA} + 4.765 \text{ mA}e^{-t/588.2 \text{ } \mu\text{s}}$$




$$v_R(0+) = 3 \text{ mA}(3.4 \text{ k}\Omega) = 10.2 \text{ V}$$

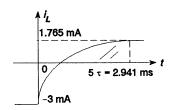
KVL: $+6 \text{ V} + 10.2 \text{ V} - v_L(0+) = 0$
 $v_L(0+) = 16.2 \text{ V}$
 $v_L = 16.2 \text{ Ve}^{-t/588.2 \text{ } \mu\text{s}}$



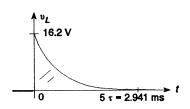

16. a.

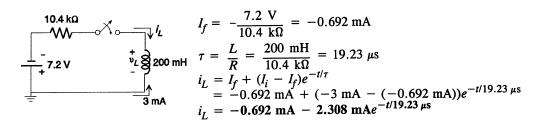


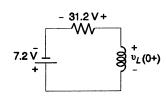


KVL:
$$-7.2 \text{ V} + 31.2 \text{ V} - v_L(0+) = 0$$

 $v_L(0+) = 24 \text{ V}$
 $v_L = 24 \text{ V}e^{-t/19.23 \,\mu\text{s}}$

b.

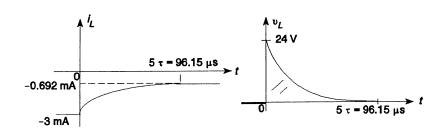

18. a.

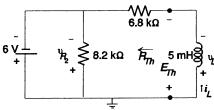

$$R_{Th} = 6.8 \text{ k}\Omega$$
$$E_{Th} = 6 \text{ V}$$

$$\tau = \frac{L}{R} = \frac{5 \text{ mH}}{6.8 \text{ k}\Omega} = 0.735 \text{ } \mu\text{s}$$

$$i_L = \frac{E}{R}(1 - e^{-t/\tau}) = \frac{6 \text{ V}}{6.8 \text{ k}\Omega}(1 - e^{-t/\tau}) = \mathbf{0.882} \times \mathbf{10^{-3}(1 - e^{-t/0.735 \,\mu\text{s}})}$$

$$v_L = Ee^{-t/\tau} = 6e^{-t/0.735 \,\mu\text{s}}$$

b. Assume steady state and $I_L = 0.882 \text{ mA}$

$$i_{L} = I_{m}e^{-t/\tau'} = 0.882 \times 10^{-3}e^{-t/0.333 \,\mu s}$$


$$i_{L} = V_{m}e^{-t/\tau'} = 0.882 \times 10^{-3}e^{-t/0.333 \,\mu s}$$


$$v_{L} = -V_{m}e^{-t/\tau'}$$

$$\sum_{C \text{ compared to defined polarity of Fig. 12.64.}} compared to defined polarity of Fig. 12.64.
$$V_{m} = I_{m}R = (0.882 \text{ mA})(15 \text{ k}\Omega) = 13.23 \text{ V}$$

$$v_{L} = -13.23 \, e^{-t/0.333 \,\mu s}$$$$


c.

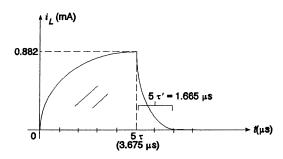

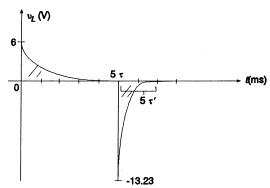

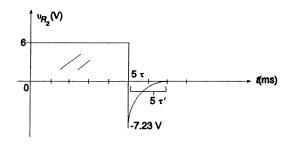d. For polarity of Fig. 12.64:

$$V_{R_{2 \text{ max}}} = I_m R_2 = (0.882 \text{ mA})(8.2 \text{ k}\Omega) = 7.23 \text{ V}$$



20.
$$i_L = 10 \text{ mA}$$
: Eq. 12.21
$$t = \tau \log_e \left(\frac{I_m}{I_m - i_L} \right) = 2 \text{ ms } \log_e \left(\frac{25 \text{ mA}}{25 \text{ mA} - 10 \text{ mA}} \right)$$
$$= 2 \text{ ms } \log_e \left(\frac{25 \text{ mA}}{15 \text{ mA}} \right) = 2 \text{ ms } \log_e 1.667$$
$$= 2 \text{ ms } (0.511)$$
$$= 1.02 \text{ ms}$$
$$v_L = 10 \text{ V}$$
: Eq. 12.22
$$t = \tau \log_e \frac{E}{v_L} = 2 \text{ ms } \log_e \frac{50 \text{ V}}{10 \text{ V}}$$
$$= 2 \text{ ms } \log_e 5 = 2 \text{ ms} (1.609)$$

22. a. Source conversion:
$$E = IR = (4 \text{ mA})(12 \text{ k}\Omega) = 48 \text{ V}$$

$$\tau = \frac{L}{R} = \frac{2 \text{ mH}}{36 \text{ k}\Omega} = 55.56 \text{ ns}$$

$$\downarrow 12 \text{ k}\Omega$$

$$\downarrow 24 \text{ k}\Omega$$

$$\downarrow 24 \text{ k}\Omega$$

$$\downarrow 24 \text{ k}\Omega$$


$$\downarrow 24 \text{ k}\Omega$$

$$i_L = \frac{E}{R}(1 - e^{-t/\tau}) = \frac{48 \text{ V}}{36 \text{ k}\Omega}(1 - e^{-t/\tau}) = 1.33 \times 10^{-3}(1 - e^{-t/55.56 \text{ ns}})$$
 $v_L = Ee^{-t/\tau} = 48e^{-t/55.56 \text{ ns}}$


b.
$$t = 100 \text{ ns}$$
:
 $i_L = 1.33 \times 10^{-3} (1 - e^{-100 \text{ ns/55.56 ns}}) = 1.33 \times 10^{-3} (1 - e^{-1.8}) = 1.11 \text{ mA}$

$$v_L = 48e^{-1.8} = 7.934 \text{ V}$$

24. a. Redrawn:

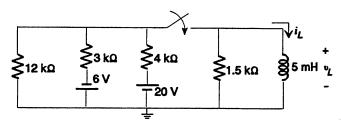

Source conversions:

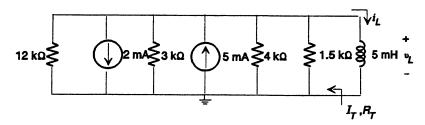

$$I_T = 5 \text{ mA} - 2 \text{ mA} = 3 \text{ mA} \dagger$$

 $\frac{1}{R_T} = \frac{1}{12 \text{ k}\Omega} + \frac{1}{3 \text{ k}\Omega} + \frac{1}{4 \text{ k}\Omega} + \frac{1}{1.5 \text{ k}\Omega} = 0.75 \text{ k}\Omega$

Source conversion:


$$E_T = I_T R_T = (3 \text{ mA})(0.75 \text{ k}\Omega) = 2.25 \text{ V}$$

$$0.75 \text{ k}\Omega$$

$$I_L = \frac{2.25 \text{ V}}{0.75 \text{ k}\Omega} (1 - e^{-t/7}) = 3 \times 10^{-3} (1 - e^{-t/6.67 \mu \text{s}})$$

$$v_L = 2.25 e^{-t/6.67 \mu \text{s}}$$

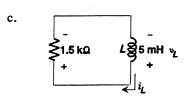b. 2τ : 0.865 I_m , 0.135 V_m i_L : 0.865 (3 mA) = **2.595** mA v_I : 0.135(2.25 V) = **0.304** V




$$\tau' = \frac{L}{R} = \frac{5 \text{ mH}}{1.5 \text{ k}\Omega} = 3.33 \text{ } \mu\text{s}$$

$$i_L = 2.595 \times 10^{-3} e^{-t/3.33 \text{ } \mu\text{s}}$$

$$i_L(0+) = 2.595 \text{ mA}$$

$$v_R(0+) = (2.595 \text{ mA})(1.5 \text{ k}\Omega) = 3.893 \text{ V}$$
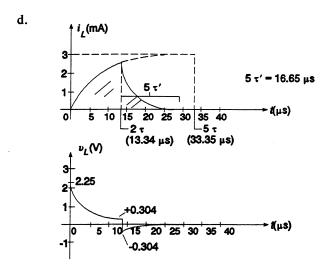
$$v_L = -3.893 \text{ V}e^{-t/3.33 \text{ } \mu\text{s}}$$



26. a.
$$i_L = \frac{E}{R_1 + R_2} e^{-t/\tau}$$
 $\tau = \frac{L}{R_T} = \frac{L}{R_1 + R_2 + R_3} = \frac{0.6 \text{ H}}{590 \Omega}$

$$= \frac{36 \text{ V}}{100 \Omega + 20 \Omega} e^{-t/1.017 \text{ ms}}$$

$$= i_L = 300 \text{ mA } e^{-t/1.017 \text{ ms}}$$

$$= 1.017 \text{m}$$

$$1 \text{ mA} = 300 \text{ mA } e^{-t/1.017 \text{ ms}}$$

$$= 3.333 \times 10^{-3} = e^{-t/1.017 \text{ ms}}$$

$$= 1.017 \text{ ms}$$

$$= 3.333 \times 10^{-3} = e^{-t/1.017 \text{ ms}}$$

$$= 5.704 = -t/1.017 \text{ ms}$$

$$= 5.704(1.017 \text{ ms}) = 5.801 \text{ ms}$$

b.
$$v_{L_{\text{max}}} = I_{L_{\text{max}}}(R_1 + R_2 + R_3) = (300 \text{ mA})(590 \Omega) = 177 \text{ V}$$

$$v_L = -177e^{-t/7} = -177e^{-t/1.017 \text{ ms}}$$

$$v_L = -177e^{-1 \text{ ms}/1.017 \text{ ms}} = -177e^{-0.983}$$


$$= -177(0.374) = -66.198 \text{ V}$$

c.
$$v_{R_3} = i_L R_3 = (300 \text{ mA } e^{-t/1.017 \text{ ms}})(20 \Omega)$$

 $= 6e^{-t/1.017 \text{ ms}} = 6e^{-5}$
 $= 6(6.738 \times 10^{-3})$
 $= 40.428 \text{ mV}$

28. a.
$$I_i = \frac{16 \text{ V}}{4.7 \text{ k}\Omega + 3.3 \text{ k}\Omega} = 2 \text{ mA}$$
 $t = 0\text{s}$: Thevenin:

 $R_{Th} = 3.3 \text{ k}\Omega + 1 \text{ k}\Omega \| 4.7 \text{ k}\Omega = 3.3 \text{ k}\Omega + 0.825 \text{ k}\Omega = 4.125 \text{ k}\Omega$
 $E_{Th} = \frac{1 \text{ k}\Omega (16 \text{ V})}{1 \text{ k}\Omega + 4.7 \text{ k}\Omega} = 2.807 \text{ V}$
 $i_L = I_f + (I_i - I_f)e^{-i/\tau}$
 $I_f = \frac{2.807 \text{ V}}{4.125 \text{ k}\Omega} = 0.680 \text{ mA}, \ \tau = \frac{L}{R} = \frac{2 \text{ H}}{4.125 \text{ k}\Omega} = 484.9 \ \mu\text{s}$
 $i_L = 0.680 \text{ mA} + (2 \text{ mA} - 0.680 \text{ mA})e^{-t/484.9 \text{ }\mu\text{s}}$
 $i_L = 0.680 \text{ mA} + 1.320 \text{ mA}e^{-t/484.9 \text{ }\mu\text{s}}$
 $v_R(0+) = 2 \text{ mA}(4.125 \text{ k}\Omega) = 8.25 \text{ V}$
 $V_C(0+): 2.807 \text{ V} - 8.25 \text{ V} - v_C = 0$
 $v_C = -5.443 \text{ V}$
 $v_C = -5.443 \text{ V}e^{-t/484.9 \text{ }\mu\text{s}}$

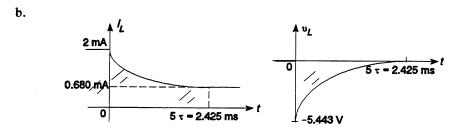

30. Source conversion:
$$I_i = \frac{18 \text{ V} + 4 \text{ V}}{1 \text{ k}\Omega + 1.2 \text{ k}\Omega} = \frac{22 \text{ V}}{2.2 \text{ k}\Omega} = 10 \text{ mA}$$

$$t = 0 + : \qquad 1 \text{ k}\Omega \longrightarrow 10 \text{ mA}$$

$$\uparrow 10 \text{ V} \longrightarrow 10 \text{ mA}$$

$$\tau = \frac{L}{R} = \frac{220 \text{ mH}}{1 \text{ k}\Omega} = 220 \text{ }\mu\text{s}$$

$$i_{L} = I_{f} + (I_{i} + I_{f})e^{-t/\tau}$$

$$= 4 \text{ mA} + (10 \text{ mA} - 4 \text{ mA})e^{-t/220 \mu s}$$

$$i_{L} = 4 \text{ mA} + 6 \text{ mA}e^{-t/220 \mu s}$$


$$v_{R}(0+) = (10 \text{ mA})(1 \text{ k}\Omega) = 10 \text{ V}$$

$$\text{KVL:} +4 \text{ V} - 10 \text{ V} - v_{L} = 0$$

$$v_{L}(0+) = -6 \text{ V}$$

$$v_{L} = -6 \text{ V}e^{-t/220 \mu s}$$

b. 10 mA /L

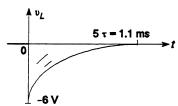


32. a.
$$L_T = 14 \text{ mH} \| 35 \text{ mH} = 10 \text{ mH}$$


$$C_T = 9 \mu \text{F} + 10 \mu \text{F} \| 90 \mu \text{F} = 9 \mu \text{F} + 9 \mu \text{F} = 18 \mu \text{F}$$

$$10 \text{ mH}$$


$$18 \mu \text{F}$$

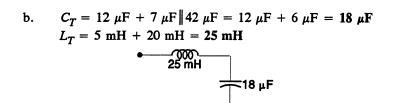

34. a.

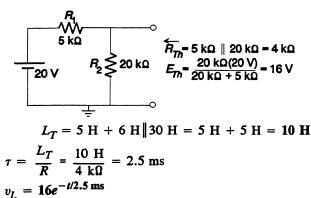
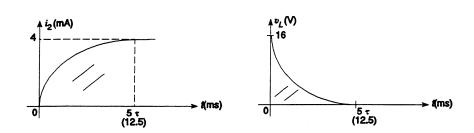
$$i_L = \frac{16 \text{ V}}{4 \text{ k}\Omega} (1 - e^{-t/\tau}) = 4 \times 10^{-3} (1 - e^{-t/2.5 \text{ ms}})$$



c.
$$v_{L_3} = \frac{v_L}{2} = 8e^{-t/2.5 \text{ ms}}$$

36.
$$I_1 = \frac{20 \text{ V}}{4 \Omega + 6 \Omega} = 2 \text{ A}, V_1 = 20 \text{ V} - I_1 4 \Omega$$

= 20 V - (2 A)(4 \Omega)
= 20 V - 8 V
= 12 V

38.
$$W_{2H} = \frac{1}{2}LI^2 = \frac{1}{2}(2 \text{ H})(4 \text{ mA})^2 = 16 \mu\text{J}$$

 $W_{3H} = \frac{1}{2}(3 \text{ H})(4 \text{ mA})^2 = 24 \mu\text{J}$

40.
$$W_{0.5\text{H}} = \frac{1}{2}(0.5 \text{ H})(2 \text{ A})^2 = 1 \text{ J}$$

 $W_{4\text{H}} = \frac{1}{2}(4 \text{ H})(4/3 \text{ A})^2 = 3.56 \text{ J}$