CHAPTER 16 (Odd)

1. a.
$$\begin{split} \mathbf{Z}_T &= j6 \ \Omega + 8 \ \Omega \ \angle -90^\circ \| \ 12 \ \Omega \ \angle -90^\circ \\ &= j6 \ \Omega + \frac{(8 \ \Omega \ \angle -90^\circ)(12 \ \Omega \ \angle -90^\circ)}{-j8\Omega - j12\Omega} = j6 \ \Omega + \frac{96 \ \Omega \ \angle -180^\circ}{20 \ \angle -90^\circ} \\ &= j6 \ \Omega + 4.8 \ \Omega \ \angle -90^\circ = j6 \ \Omega - j4.8 \ \Omega \\ \mathbf{Z}_T &= j1.2 \ \Omega = \mathbf{1.2} \ \Omega \ \angle 90^\circ \end{split}$$

b.
$$I = \frac{E}{Z_T} = \frac{12 \text{ V } \angle 0^{\circ}}{1.2 \Omega \angle 90^{\circ}} = 10 \text{ A } \angle -90^{\circ}$$

c.
$$I_1 = I = 10 \text{ A } \angle -90^{\circ}$$

d. (CDR)
$$I_{2} = \frac{(12 \Omega \angle -90^{\circ})(10 A \angle -90^{\circ})}{-j12 \Omega - j8\Omega} = \frac{120 A \angle -180^{\circ}}{20 \angle -90^{\circ}} = 6 A \angle -90^{\circ}$$

$$I_{3} = \frac{(8 \Omega \angle -90^{\circ})(10 A \angle -90^{\circ})}{20 \Omega \angle -90^{\circ}} = \frac{80 A \angle -180^{\circ}}{20 \angle -90^{\circ}} = 4 A \angle -90^{\circ}$$

e.
$$V_L = (I \ \angle \theta)(X_L \ \angle 90^\circ) = (10 \ A \ \angle -90^\circ)(6 \ \Omega \ \angle 90^\circ) = 60 \ V \ \angle 0^\circ$$

3. a.
$$\begin{split} \mathbf{Z}_T &= 4.7 \ \Omega \, \big\| \, (9.1 \ \Omega - j12 \ \Omega) = 4.7 \ \Omega \, \angle \, 0^{\circ} \, \big\| \, 15.06 \ \Omega \, \angle \, -52.826^{\circ} \\ &= \frac{70.782 \ \Omega \, \angle \, -52.826^{\circ}}{4.7 \, + \, 9.1 \, - j12} = \frac{70.782 \ \Omega \, \angle \, -52.826^{\circ}}{13.8 \, - j12} \\ &= \frac{70.782 \ \Omega \, \angle \, -52.826^{\circ}}{18.288 \ \angle \, -41.009^{\circ}} = 3.87 \ \Omega \, \angle \, -11.817^{\circ} \\ \mathbf{Y}_T &= \frac{1}{\mathbf{Z}_T} = \frac{1}{3.87 \ \Omega \, \angle \, -11.817^{\circ}} = \mathbf{0.258 \ S} \ \angle \, \mathbf{11.817^{\circ}} \end{split}$$

b.
$$I_s = \frac{E}{Z_T} = \frac{60 \text{ V } \angle 30^{\circ}}{3.87 \Omega \angle -11.817^{\circ}} = 15.504 \text{ A } \angle 41.871^{\circ}$$

c. (CDR)
$$I_2 = \frac{(4.7 \ \Omega \ \angle 0^\circ)(15.504 \ A \ \angle 41.817^\circ)}{4.7 \ \Omega + 9.1 \ \Omega - j12 \ \Omega} = \frac{72.869 \ A \ \angle 41.817^\circ}{18.288 \ \angle -41.009^\circ}$$
$$= 3.985 \ A \ \angle 82.826^\circ$$

d. (VDR)
$$V_C = \frac{(12 \Omega \angle -90^\circ)(60 \text{ V } \angle 30^\circ)}{9.1 \Omega - j12 \Omega} = \frac{720 \text{ V } \angle -60^\circ}{15.06 \angle -52.826^\circ} = 47.809 \text{ V } \angle -7.174^\circ$$

e.
$$P = EI \cos \theta = (60 \text{ V})(15.504 \text{ A})\cos(41.87^{\circ} - 30^{\circ})$$

= 930.24(0.979) = 910.71 W

5. a.
$$400 \Omega \angle -90^{\circ} \| 400 \Omega \angle -90^{\circ} = \frac{400 \Omega \angle -90^{\circ}}{2} = 200 \Omega \angle -90^{\circ}$$

 $\mathbf{Z}' = 200 \Omega - j200 \Omega = 282.843 \Omega \angle -45^{\circ}$
 $\mathbf{Z}'' = 560 \Omega + j560 \Omega = 791.960 \Omega \angle 45^{\circ}$


$$\begin{split} \mathbf{Z}_T &= \mathbf{Z}' \, \| \, \mathbf{Z}'' \, = \, \frac{(282.843 \, \Omega \, \angle -45^\circ)(791.960 \, \Omega \, \angle 45^\circ)}{(200 \, \Omega \, - j200 \, \Omega) \, + (560 \, \Omega \, + j560 \, \Omega)} \\ &= \, \frac{224,000.34 \, \Omega \, \angle 0^\circ}{840.952 \, \angle 25.346^\circ} \, = \, \mathbf{266.365 \, \Omega} \, \, \angle \, -\mathbf{25.346}^\circ \\ \mathbf{I} &= \, \frac{\mathbf{E}}{\mathbf{Z}_T} \, = \, \frac{100 \, \, \mathbf{V} \, \angle 0^\circ}{266.365 \, \Omega \, \angle -25.346^\circ} \, = \, \mathbf{0.375 \, A} \, \, \angle \, \mathbf{25.346}^\circ \end{split}$$

b.
$$V_C = \frac{(200 \ \Omega \ \angle -90^\circ)(100 \ V \ \angle 0^\circ)}{200 \ \Omega - j200 \ \Omega} = \frac{20,000 \ V \ \angle -90^\circ}{282.843 \ \angle -45^\circ} = 70.711 \ V \ \angle -45^\circ$$

c.
$$P = EI \cos \theta = (100 \text{ V})(0.375 \text{ A}) \cos 25.346^{\circ}$$

= $(37.5)(0.904) = 33.9 \text{ W}$

7. a.

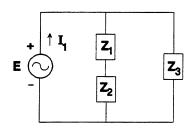

$$Z_{1} = 10 \Omega \angle 0^{\circ}$$

$$Z_{2} = 80 \Omega \angle 90^{\circ} \| 20 \Omega \angle 0^{\circ}$$

$$= \frac{1600 \Omega \angle 90^{\circ}}{20 + j80} = \frac{1600 \Omega \angle 90^{\circ}}{82.462 \angle 75.964^{\circ}}$$

$$= 19.403 \Omega \angle 14.036^{\circ}$$

$$Z_{3} = 60 \Omega \angle -90^{\circ}$$


$$\begin{split} \mathbf{Z}_T &= (\mathbf{Z}_1 + \mathbf{Z}_2) \, \| \, \mathbf{Z}_3 \\ &= (10 \, \Omega + 18.824 \, \Omega + j4.706 \, \Omega) \, \| \, 60 \, \Omega \, \angle -90^{\circ} \\ &= 29.206 \, \Omega \, \angle 9.273^{\circ} \, \| \, 6\Omega \, \angle -90^{\circ} = \frac{1752.36 \, \Omega \, \angle -80.727^{\circ}}{28.824 \, + j4.706 \, - j60} \\ &= \frac{1752.36 \, \Omega \, \angle -80.727^{\circ}}{62.356 \, \angle -62.468^{\circ}} = 28.103 \, \Omega \, \angle -18.259^{\circ} \\ \mathbf{I}_1 &= \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{40 \, \mathrm{V} \, \angle 0^{\circ}}{28.103 \, \Omega \, \angle -18.259^{\circ}} = 1.423 \, \mathrm{A} \, \angle \, 18.259^{\circ} \end{split}$$

b.
$$V_1 = \frac{Z_2E}{Z_2 + Z_1} = \frac{(19.403 \Omega \angle 14.036^\circ)(40 \text{ V } \angle 0^\circ)}{29.206 \Omega \angle 9.273^\circ} = \frac{776.12 \text{ V } \angle 14.036^\circ}{29.206 \angle 9.273^\circ} = 26.574 \text{ V } \angle 4.763^\circ$$

c.
$$P = EI \cos \theta = (40 \text{ V})(1.423 \text{ A})\cos 18.259^{\circ}$$

= **54.074** W

9. a.

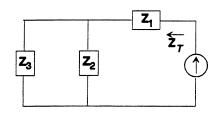

$$Z' = 3 \Omega \angle 0^{\circ} \| 4 \Omega \angle -90^{\circ} = \frac{12 \Omega \angle -90^{\circ}}{3 - j4}$$

$$= \frac{12 \Omega \angle -90^{\circ}}{5 \angle -53.13^{\circ}} = 2.4 \Omega \angle -36.87^{\circ}$$

$$Z_{3} = 2 Z' + j7 \Omega$$

$$= 4.8 \Omega \angle -36.87^{\circ} + j7 \Omega$$

$$= 3.84 \Omega - j2.88 \Omega + j7 \Omega$$

$$= 3.84 \Omega + j4.12 \Omega$$

$$= 5.632 \Omega \angle 47.015^{\circ}$$

$$\begin{split} \mathbf{Z}_T &= \ \mathbf{Z}_1 \ + \ \mathbf{Z}_2 \ \| \ \mathbf{Z}_3 \ = \ 6.8 \ \Omega \ + \ 8.2 \ \Omega \ \angle 0^\circ \| \ 5.632 \ \Omega \ \angle 47.015^\circ \\ &= \ 6.8 \ \Omega \ + \ \frac{46.182 \ \Omega \ \angle 47.015^\circ}{8.2 \ + \ 3.84 \ + \ j4.12} \ = \ 6.8 \ \Omega \ + \ \frac{46.182 \ \Omega \ \angle 47.015^\circ}{12.725 \ \angle 18.891^\circ} \\ &= \ 6.8 \ \Omega \ + \ 3.629 \ \Omega \ \angle 28.124^\circ = \ 6.8 \ \Omega \ + \ 3.201 \ \Omega \ + \ j1.711 \ \Omega \\ &= \ 10 \ \Omega \ + \ j1.711 \ \Omega \ = \ 10.145 \ \Omega \ \angle 9.709^\circ \end{split}$$

$$\mathbf{Y}_T = \ \frac{1}{\mathbf{Z}_T} \ = \ \mathbf{0.099} \ \mathbf{S} \ \angle \ - \mathbf{9.709}^\circ \end{split}$$

b.
$$V_1 = IZ_1 = (3 \text{ A } \angle 30^\circ)(6.8 \Omega \angle 0^\circ) = 20.4 \text{ V } \angle 30^\circ$$

 $V_2 = I(Z_2 || Z_3) = (3 \text{ A } \angle 30^\circ)(3.629 \Omega \angle 28.124^\circ)$
 $= 10.887 \text{ V } \angle 58.124^\circ$

c.
$$I_3 = \frac{V_2}{Z_3} = \frac{10.877 \text{ V } \angle 58.124^{\circ}}{5.632 \Omega \angle 47.015^{\circ}} = 1.933 \text{ A } \angle 11.109^{\circ}$$

$$Z_1 = 2 \Omega - j2 \Omega = 2.828 \Omega \angle -45^{\circ}$$

$$Z_2 = 3 \Omega - j9 \Omega + j6 \Omega$$

$$= 3 \Omega - j3 \Omega = 4.243 \Omega \angle -45^{\circ}$$

$$Z_3 = 10 \Omega \angle 0^{\circ}$$

$$\begin{split} \mathbf{Y}_T &= \ \frac{1}{\mathbf{Z}_1} \ + \ \frac{1}{\mathbf{Z}_2} \ + \ \frac{1}{\mathbf{Z}_3} \ = \ \frac{1}{2.828 \ \Omega \ \angle -45^\circ} \ + \ \frac{1}{4.243 \ \Omega \ \angle -45^\circ} \ + \ \frac{1}{10 \ \Omega \ \angle 0^\circ} \\ &= 0.354 \ \mathbf{S} \ \angle 45^\circ \ + \ 0.236 \ \mathbf{S} \ \angle 45^\circ \ + \ 0.1 \ \mathbf{S} \ \angle 0^\circ \ = \ 0.59 \ \mathbf{S} \ \angle 45^\circ \ + \ 0.1 \ \mathbf{S} \ \angle 0^\circ \\ &= 0.417 \ \mathbf{S} \ + \ j \ 0.417 \ \mathbf{S} \ + \ 0.1 \ \mathbf{S} \\ \mathbf{Y}_T &= 0.517 \ \mathbf{S} \ + \ j \ 0.417 \ \mathbf{S} \ = \ 0.664 \ \mathbf{S} \ \angle 38.889^\circ \\ \mathbf{Z}_T &= \ \frac{1}{\mathbf{Y}_T} \ = \ \frac{1}{0.664 \ \mathbf{S} \ \angle 38.889^\circ} \ = \ \mathbf{1.506 \ \Omega} \ \angle \ -38.889^\circ \\ \mathbf{I} &= \ \frac{\mathbf{E}}{\mathbf{Z}_T} \ = \ \frac{50 \ \mathbf{V} \ \angle 0^\circ}{1.506 \ \Omega \ \angle -38.889^\circ} \ = \ \mathbf{33.201 \ A} \ \angle \ 38.889^\circ \end{split}$$

13.
$$R_3 + R_4 = 2.7 \text{ k}\Omega + 4.3 \text{ k}\Omega = 7 \text{ k}\Omega$$

 $R' = 3 \text{ k}\Omega || 7 \text{ k}\Omega = 2.1 \text{ k}\Omega$
 $Z' = 2.1 \text{ k}\Omega - j10 \Omega$

(CDR) I' (of 10
$$\Omega$$
 cap.) = $\frac{(40 \text{ k}\Omega \angle 0^{\circ})(20 \text{ mA } \angle 0^{\circ})}{40 \text{ k}\Omega + 2.1 \text{ k}\Omega - j10 \Omega}$
= 19 mA $\angle +0.014^{\circ}$ as expected since $R_1 \gg \mathbf{Z}'$

(CDR)
$$I_4 = \frac{(3 \text{ k}\Omega \text{ } \angle 0^\circ)(19 \text{ mA } \angle 0.014^\circ)}{3 \text{ k}\Omega + 7 \text{ k}\Omega} = \frac{57 \text{ mA } \angle 0.014^\circ}{10}$$
$$= 5.7 \text{ mA } \angle 0.014^\circ$$
$$P = I^2 R = (5.7 \text{ mA})^2 4.3 \text{ k}\Omega = 139.71 \text{ mW}$$

CHAPTER 16 (Even)

2. a.
$$\mathbf{Z}_{T} = 3 \Omega + j6 \Omega + 2 \Omega \angle 0^{\circ} \| 8 \Omega \angle -90^{\circ}$$

= $3 \Omega + j6 \Omega + 1.94 \Omega \angle -14.04^{\circ}$
= $3 \Omega + j6 \Omega + 1.882 \Omega - j0.471 \Omega$
= $4.882 \Omega + j5.529 \Omega = 7.376 \Omega \angle 48.556^{\circ}$

b.
$$I_s = \frac{E}{Z_T} = \frac{30 \text{ V } \angle 0^{\circ}}{7.376 \Omega \angle 48.556^{\circ}} = 4.067 \text{ A } \angle -48.556^{\circ}$$

c.
$$I_C = \frac{\mathbf{Z}_{R_2} \mathbf{I}_s}{\mathbf{Z}_{R_2} + \mathbf{Z}_C} = \frac{(2 \Omega \angle 0^\circ)(4.067 \text{ A} \angle -48.556^\circ)}{2 \Omega - j8 \Omega}$$
$$= \frac{8.134 \text{ A} \angle -48.556^\circ}{8.246 \angle -75.964^\circ} = \mathbf{0.986 \text{ A}} \angle 27.408^\circ$$

d.
$$V_L = \frac{Z_L E}{Z_T} = \frac{(6 \Omega \angle 90^\circ)(30 \text{ V} \angle 0^\circ)}{7.376 \Omega \angle 48.556^\circ} = \frac{180 \text{ V} \angle 90^\circ}{7.376 \angle 48.556^\circ}$$

= 24.403 V \angle 41.44°

4. a.
$$\mathbf{Z}_{T} = 2 \Omega + \frac{(4 \Omega \angle -90^{\circ})(6\Omega \angle 90^{\circ})}{-j4 \Omega + j6 \Omega} + \frac{4 \Omega \angle 0^{\circ})(3 \Omega \angle 90^{\circ})}{4 \Omega + j3 \Omega}$$

$$= 2 \Omega + \frac{24 \Omega \angle 0^{\circ}}{2 \angle 90^{\circ}} + \frac{12 \Omega \angle 90^{\circ}}{5 \angle 36.87^{\circ}}$$

$$= 2 \Omega + 12 \Omega \angle -90^{\circ} + 2.4 \angle 53.13^{\circ}$$

$$= 2 \Omega - j12 \Omega + 1.44 \Omega + j1.92 \Omega$$

$$= 3.44 \Omega - j10.08 \Omega = 10.65 \Omega \angle -71.16^{\circ}$$

b.
$$V_2 = I(2.4 \Omega \angle 53.13^\circ) = (5 A \angle 0^\circ)(2.4 \Omega \angle 53.13^\circ) = 12 V \angle 53.13^\circ$$

 $I_L = \frac{(4 \Omega \angle 0^\circ)(I)}{4 \Omega + j3 \Omega} = \frac{(4 \Omega \angle 0^\circ)(5 A \angle 0^\circ)}{5 \Omega \angle 36.87^\circ} = \frac{20 A \angle 0^\circ}{5 \angle 36.87^\circ} = 4 A \angle -36.87^\circ$

c.
$$F_p = \frac{R}{Z_T} = \frac{3.44 \ \Omega}{10.65 \ \Omega} = 0.323$$
 (leading)

6. a.
$$\mathbf{Z}_1 = 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^{\circ}$$

 $\mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}_1} = \frac{120 \text{ V } \angle 60^{\circ}}{5 \Omega \angle 53.13^{\circ}} = 24 \text{ A } \angle 6.87^{\circ}$

b.
$$V_C = \frac{(13 \Omega \angle -90^\circ)(120 \text{ V} \angle 60^\circ)}{-j13 \Omega + j7 \Omega} = \frac{1560 \text{ V} \angle -30^\circ}{6 \angle -90^\circ} = 260 \text{ V} \angle 60^\circ$$

c.
$$V_{R_1} = (I_1 \angle \theta)R \angle 0^\circ = (24 \text{ A } \angle 6.87^\circ)(3 \Omega \angle 0^\circ) = 72 \text{ V } \angle 6.87^\circ$$

$$V_{ab} + V_{R_1} - V_C = 0$$

$$V_{ab} = V_C - V_{R_1} = 260 \text{ V } \angle 60^\circ - 72 \text{ V } \angle 6.87^\circ$$

$$= (130 \text{ V } + j225.167 \text{ V}) - (71.483 \text{ V } + j8.612 \text{ V})$$

$$= 58.517 \text{ V } + j216.555 \text{ V } = 224.32 \text{ V } \angle 74.88^\circ$$

8. a.
$$Z_1 = 2 \Omega + j1 \Omega = 2.236 \Omega \angle 26.565^{\circ}, Z_2 = 3 \Omega \angle 0^{\circ}$$

$$Z_3 = 16 \Omega + j15 \Omega - j7 \Omega = 16 \Omega + j8 \Omega = 17.889 \Omega \angle 26.565^{\circ}$$

$$Y_T = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{2.236 \Omega \angle 26.565^{\circ}} + \frac{1}{3 \Omega \angle 0^{\circ}} + \frac{1}{17.889 \Omega \angle 26.565^{\circ}}$$

$$= 0.447 \text{ S } \angle -26.565^{\circ} + 0.333 \text{ S } \angle 0^{\circ} + 0.056 \text{ S } \angle -26.565^{\circ}$$

$$= (0.4 \text{ S} - j0.2 \text{ S}) + (0.333 \text{ S}) + (0.05 \text{ S} - j0.025 \text{ S})$$

$$= 0.783 \text{ S} - j0.225 \text{ S} = 0.815 \text{ S } \angle -16.032^{\circ}$$

$$Z_T = \frac{1}{Y_T} = \frac{1}{0.815 \text{ S } \angle -16.032^{\circ}} = 1.227 \Omega \angle 16.032^{\circ}$$

b.
$$I_1 = \frac{E}{Z_1} = \frac{60 \text{ V } \angle 0^{\circ}}{2.236 \Omega \angle 26.565^{\circ}} = 26.834 \text{ A } \angle -26.565^{\circ}$$

$$I_2 = \frac{E}{Z_2} = \frac{60 \text{ V } \angle 0^{\circ}}{3 \Omega \angle 0^{\circ}} = 20 \text{ A } \angle 0^{\circ}$$

$$I_3 = \frac{E}{Z_3} = \frac{60 \text{ V } \angle 0^{\circ}}{17.889 \Omega \angle 26.565^{\circ}} = 3.354 \text{ A } \angle -26.565^{\circ}$$

c.
$$I_s = \frac{E}{Z_T} = \frac{60 \text{ V } \angle 0^{\circ}}{1.227 \Omega \angle 16.032^{\circ}} = 48.9 \text{ A } \angle -16.032^{\circ}$$

$$I_s \stackrel{?}{=} I_1 + I_2 + I_3$$

48.9 A
$$\angle -16.032^{\circ} \stackrel{?}{=} 26.834$$
 A $\angle -26.565^{\circ} + 20$ A $\angle 0^{\circ} + 3.354$ A $\angle -26.565^{\circ}$
= $(24 \text{ A} - j12 \text{ A}) + (20 \text{ A}) + (3 \text{ A} - j1.5 \text{ A})$
= $47 \text{ A} + j13.5$ A = 48.9 A $\angle -16.026^{\circ}$ (checks)

d.
$$F_p = \frac{G}{Y_T} = \frac{0.783 \text{ A}}{0.815 \text{ S}} = 0.961 \text{ (lagging)}$$

10. a.
$$X_{L_1} = \omega L_1 = 2\pi (10^3 \text{ Hz})(0.1 \text{ H}) = 628 \Omega$$

$$X_{L_2} = \omega L_2 = 2\pi (10^3 \text{ Hz})(0.2 \text{ H}) = 1.256 \text{ k}\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi (10^3 \text{ Hz})(1 \text{ }\mu\text{F})} = 0.159 \text{ k}\Omega$$

$$Z_T = R \angle 0^\circ + X_{L_1} \angle 90^\circ + X_C \angle -90^\circ \| X_{L_2} \angle 90^\circ$$

$$= 300 \Omega + j628 \Omega + 0.159 \text{ k}\Omega \angle -90^\circ \| 1.256 \text{ k}\Omega \angle 90^\circ$$

$$= 300 \Omega + j628 \Omega - j182 \Omega$$

$$= 300 \Omega + j446 \Omega = 537.51 \Omega \angle 56.07^\circ$$

$$Y_T = \frac{1}{Z_T} = \frac{1}{537.51 \Omega \angle 56.07^\circ} = 1.86 \text{ mS } \angle -56.07^\circ$$

b.
$$I_s = \frac{E}{Z_T} = \frac{50 \text{ V } \angle 0^{\circ}}{537.51 \Omega \angle 56.07^{\circ}} = 93 \text{ mA } \angle -56.07^{\circ}$$

c. (CDR):
$$I_{1} = \frac{\mathbf{Z}_{L_{2}}\mathbf{I}_{s}}{\mathbf{Z}_{L_{2}} + \mathbf{Z}_{C}} = \frac{(1.256 \text{ k}\Omega \angle 90^{\circ})(93 \text{ mA} \angle -56.07^{\circ})}{+j1.256 \text{ k}\Omega - j0.159 \text{ k}\Omega}$$

$$= \frac{116.81 \text{ mA} \angle 33.93^{\circ}}{1.097 \angle 90^{\circ}} = 106.48 \text{ mA} \angle -56.07^{\circ}$$

$$I_{2} = \frac{\mathbf{Z}_{C}\mathbf{I}_{s}}{\mathbf{Z}_{L_{2}} + \mathbf{Z}_{C}} = \frac{(0.159 \text{ k}\Omega \angle -90^{\circ})(93 \text{ mA} \angle -56.07^{\circ})}{1.097 \text{ k}\Omega \angle 90^{\circ}}$$

$$= \frac{14.79 \text{ mA} \angle -146.07^{\circ}}{1.097 \angle 90^{\circ}} = 13.48 \text{ mA} \angle -236.07^{\circ}$$

$$= 13.48 \text{ mA} \angle 123.93^{\circ}$$

d.
$$V_1 = (I_2 \angle \theta)(X_{L_2} \angle 90^\circ) = (13.48 \text{ mA } \angle 123.92^\circ)(1.256 \text{ k}\Omega \angle 90^\circ)$$

 $= 16.931 \text{ V } \angle 213.93^\circ$
 $V_{ab} = \mathbf{E} - (I_s \angle \theta)(R \angle 0^\circ) = 50 \text{ V } \angle 0^\circ - (93 \text{ mA } \angle -56.07^\circ)(300 \Omega \angle 0^\circ)$
 $= 50 \text{ V} - 27.9 \text{ V } \angle -56.07^\circ$
 $= 50 \text{ V} - (15.573 \text{ V} - j23.149 \text{ V})$
 $= 34.43 \text{ V} + j23.149 \text{ V} = 41.49 \text{ V } \angle 33.92^\circ$

e.
$$P = I_s^2 R = (93 \text{ mA})^2 300 \Omega = 2.595 \text{ W}$$

f.
$$F_p = \frac{R}{Z_T} = \frac{300 \Omega}{537.51 \Omega} = 0.558 \text{ (lagging)}$$

12.
$$\mathbf{Z}' = 12 \Omega - j20 \Omega = 23.324 \Omega \angle -59.036^{\circ}$$
 $R_4 \angle 0^{\circ} \| \mathbf{Z}' = 20 \Omega \angle 0^{\circ} \| 23.324 \Omega \angle -59.036^{\circ} = 12.362 \Omega \angle -27.031^{\circ}$
 $\mathbf{Z}'' = R_3 \angle 0^{\circ} + R_4 \angle 0^{\circ} \| \mathbf{Z}' = 12 \Omega + 12.362 \Omega \angle -27.031^{\circ}$
 $= 12 \Omega + (11.012 \Omega - j5.618 \Omega)$
 $= 23.012 \Omega - j5.618 \Omega = 23.688 \Omega \angle -13.719^{\circ}$
 $R_2 \angle 0^{\circ} \| \mathbf{Z}'' = 20 \Omega \angle 0^{\circ} \| 23.688 \Omega \angle -13.719^{\circ} = 10.922 \Omega \angle -6.277^{\circ}$
 $\mathbf{Z}_T = R_1 \angle 0^{\circ} + R_2 \angle 0^{\circ} \| \mathbf{Z}'' = 12 \Omega + 10.922 \Omega \angle -6.277^{\circ}$
 $= 12 \Omega + (10.857 \Omega - j1.194 \Omega)$
 $= 22.857 \Omega - j1.194 \Omega = 22.888 \Omega \angle -2.99^{\circ}$
 $\mathbf{I}_S = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{100 \mathbf{V} \angle 0^{\circ}}{22.888 \Omega \angle -2.99^{\circ}} = 4.371 \mathbf{A} \angle 2.99^{\circ}$
 $\mathbf{I}_{R_1} = \mathbf{I}$
 $\mathbf{I}_{R_3} = \frac{R_2 \angle 0^{\circ} \mathbf{I}_S}{R_2 \angle 0^{\circ} + \mathbf{Z}''} = \frac{(20 \Omega \angle 0^{\circ})(4.371 \mathbf{A} \angle 2.99^{\circ})}{20 \Omega + 23.012 \Omega - j5.618 \Omega} = \frac{87.42 \mathbf{A} \angle 2.99^{\circ}}{43.377 \angle -7.442^{\circ}}$
 $= 2.015 \mathbf{A} \angle 10.432^{\circ}$

$$I_{5} = \frac{R_{4} \angle 0^{\circ} I_{R_{3}}}{R_{4} \angle 0^{\circ} + \mathbf{Z}'} = \frac{(20 \Omega \angle 0^{\circ})(2.015 \text{ A} \angle 10.432^{\circ})}{20 \Omega + 12 \Omega - j20 \Omega} = \frac{40.3 \text{ A} \angle 10.432^{\circ}}{37.736 \angle -32.005^{\circ}}$$
$$= 1.068 \text{ A} \angle 42.437^{\circ}$$

14.
$$Z' = X_{C_2} \angle -90^{\circ} \| R_1 \angle 0^{\circ} = 2 \Omega \angle -90^{\circ} \| 1 \Omega \angle 0^{\circ}$$

$$= \frac{2 \Omega \angle -90^{\circ}}{1 - j2} = \frac{2 \Omega \angle -90^{\circ}}{2.236 \angle -63.435^{\circ}}$$

$$= 0.894 \Omega \angle -26.565^{\circ}$$

$$Z'' = X_{L_2} \angle 90^{\circ} + Z' = +j8 \Omega + 0.894 \Omega \angle -26.565^{\circ}$$

$$= +j8 \Omega + (0.8 \Omega - j4 \Omega)$$

$$= 0.8 \Omega + j4 = 4.079 \Omega \angle 78.69^{\circ}$$

$$I_{X_{L_2}} = \frac{X_{C_1} \angle -90^{\circ} I}{X_{C_1} \angle -90^{\circ} + Z''} = \frac{2 \Omega(\angle -90^{\circ})(0.5 \text{ A } \angle 0^{\circ})}{-j2 \Omega + (0.8 \Omega + j4 \Omega)} = \frac{1 \text{A } \angle -90^{\circ}}{0.8 + j2}$$

$$= \frac{1 \text{ A } \angle -90^{\circ}}{2.154 \angle 68.199^{\circ}} = 0.464 \text{ A } \angle -158.99^{\circ}$$

$$I_1 = \frac{X_{C_2} \angle -90^{\circ} I_{X_{L_2}}}{X_{C_2} \angle -90^{\circ} + R_1} = \frac{(2 \Omega \angle -90^{\circ})(0.464 \text{ A } \angle -158.99^{\circ})}{-j2 \Omega + 1 \Omega} = \frac{0.928 \text{ A } \angle -248.99^{\circ}}{2.236 \angle -63.435^{\circ}}$$

$$= 0.415 \text{ A } \angle 174.45^{\circ}$$